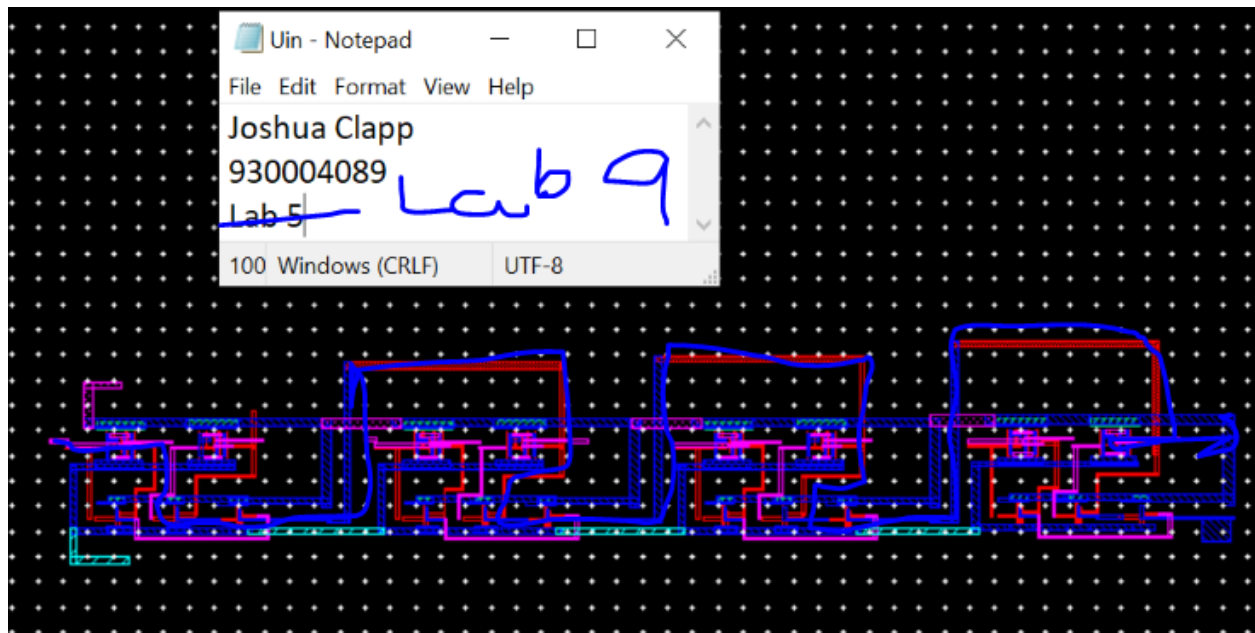


Joshua Clapp

Instead of recreating the whole lab using transistor level, I modified the symbols with the shown transistors and resimulated. This LAYOUT not schematic best showed the actual work I did since the shows nmos and pmos paths, not the recalculated values.

Layout:



Critical path is: xor0 -> nand0 -> nand0 -> nand1 -> nand1 -> nand2 -> nand2 -> xor3

Critical path:

adder0 = $(4 * 4/3 * 4/3)$ path xor -> nand -> nand

adder1 = $(4/3 * 4/3)$ path nand -> nand

adder2 = $(4/3 * 4/3)$ path nand -> nand

adder3 = (4) path xor

Unused Brach paths:

adder0 = (4) path xor

adder1 = (4) path xor

adder2 = (4) path xor

adder3 = $(4/3)$ path nand

G (Logical Effort Path) = 89.898

H (Electrical Effort Path) = 30 fF / 9.85 fF = 3.05

B (Branching Effort Path) = 85.333

F (Logical * Electrical * Branching) = 23364.35

N = 8

$f(\text{hat}) = (GBH)^{(1/N)} = 3.52$

Delays:

Case	Pins	Non Optimized	Optimized	Improvement
A=0000	Sum 0	6600	921	12.24571201
B=1111	Sum 1	9451	970	9.308127819
Carry In=1	Sum 2	1021	1062	50.98415747
	Sum 3	1061	1074	50.30444965
	Carry	985	981	49.8982706
A=1010	Sum 0	662	921	58.18066961
B=0101	Sum 1	1112	1065	48.92053284
Carry In=0	Sum 2	1025	1002	49.4326591
	Sum 3	1023	1000	49.43153732
	Carry	985	993	50.20222447
A=1010	Sum 0	663	921	58.14393939
B=0101	Sum 1	945	982	50.96004152
Carry In=1	Sum 2	1025	1014	49.73025993
	Sum 3	1063	1032	49.2601432
	Carry	1258	1086	46.33105802
A=1100	Sum 0	702	923	56.8
B=1000	Sum 1	709	952	57.31487056
Carry In=0	Sum 2	1036	1052	50.38314176
	Sum 3	750	931	55.38370018
	Carry	1584	1071	40.33898305

Power consumptions:


Case	Non-optimized (uW)	Optimized (uW)	Improvement
A=0000, B=1111, Carry In= 1	-330.8	-87.6	20.93690249
A=1010,B=0101, Carry In= 0	-472	-86.2	15.44249373
A=1010, B=0101, Carry In=1	-330.8	-86.47	20.7227934
A=1100, B=1000, Carry In=0	-457.625	-88.9	16.2664105

Area:


Non-optimized (u ² m ²)	Optimized (u ² m ²)
8800000	17440000

Proof


Case 1 screenshot

 


Case 2 screen shot

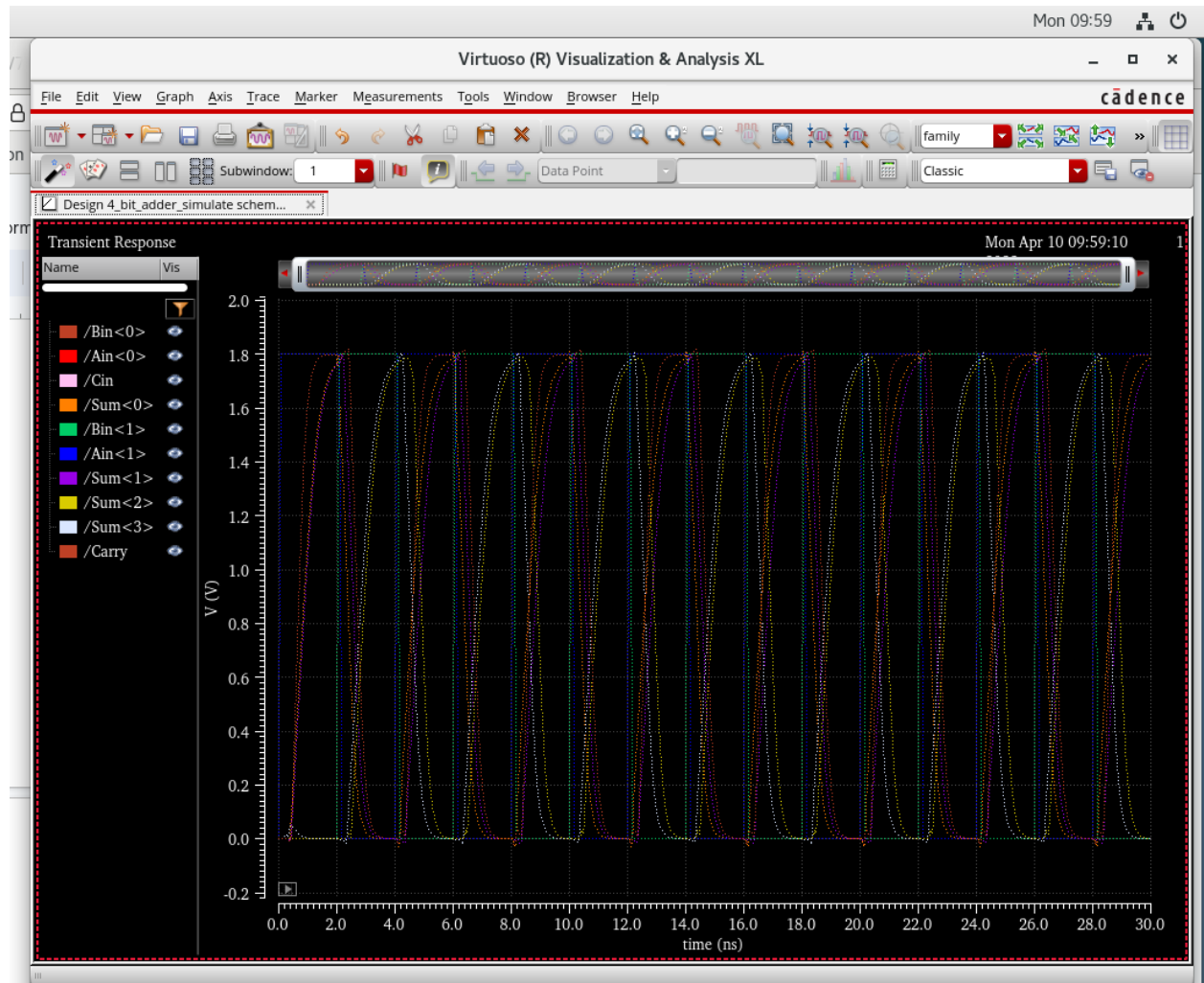


Case 3 screenshot

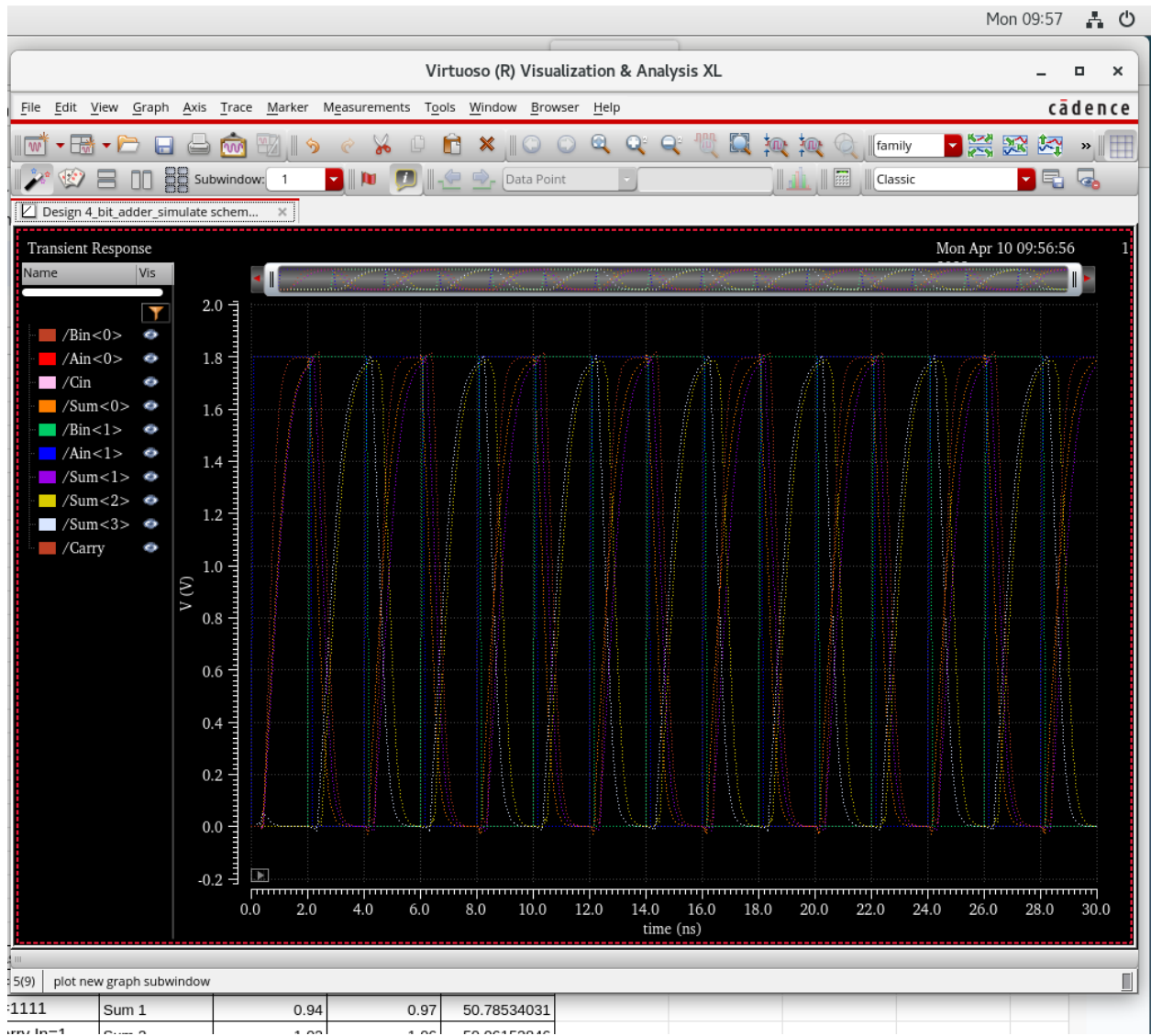


Case 4 screenshot

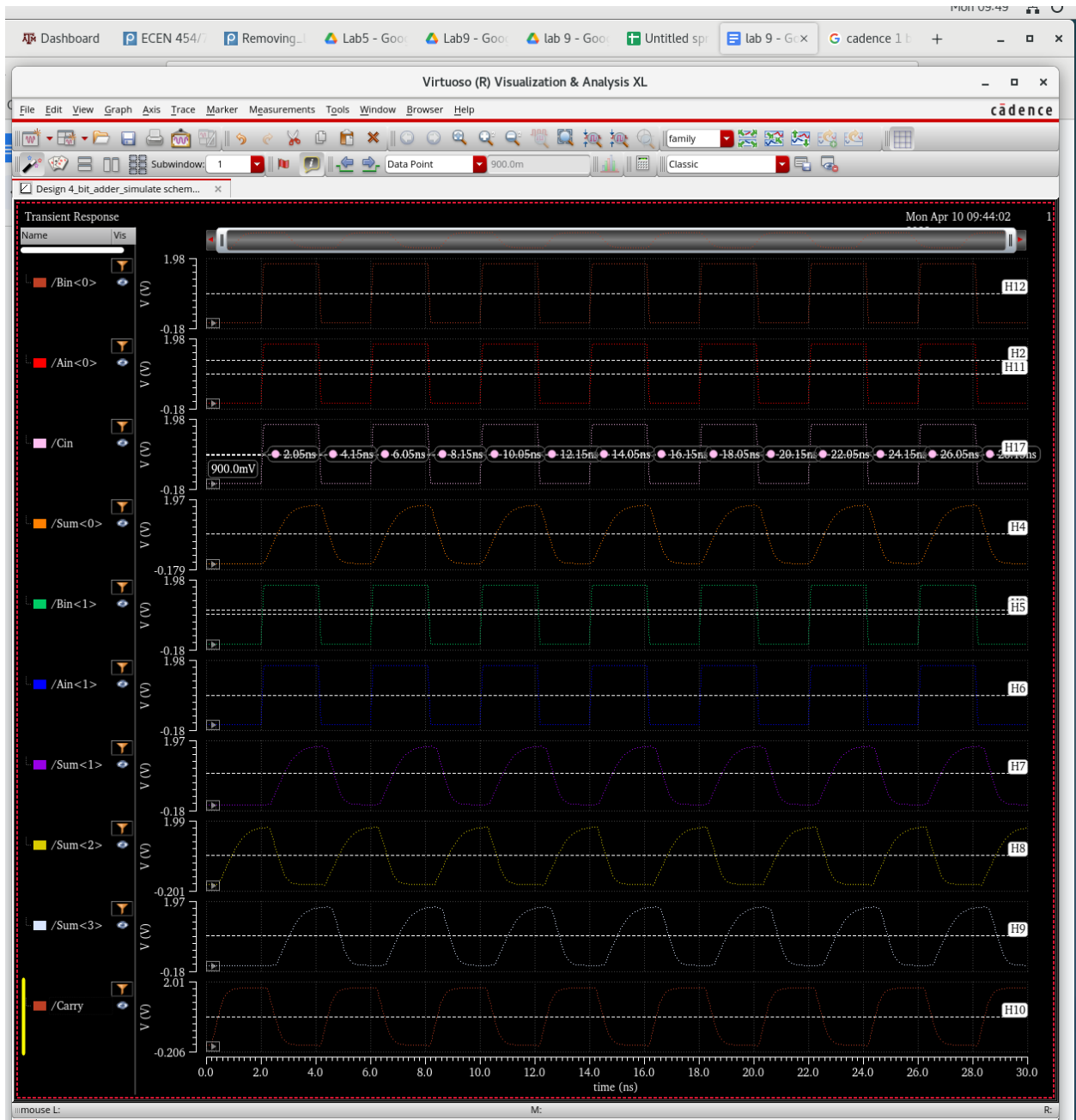


Xor

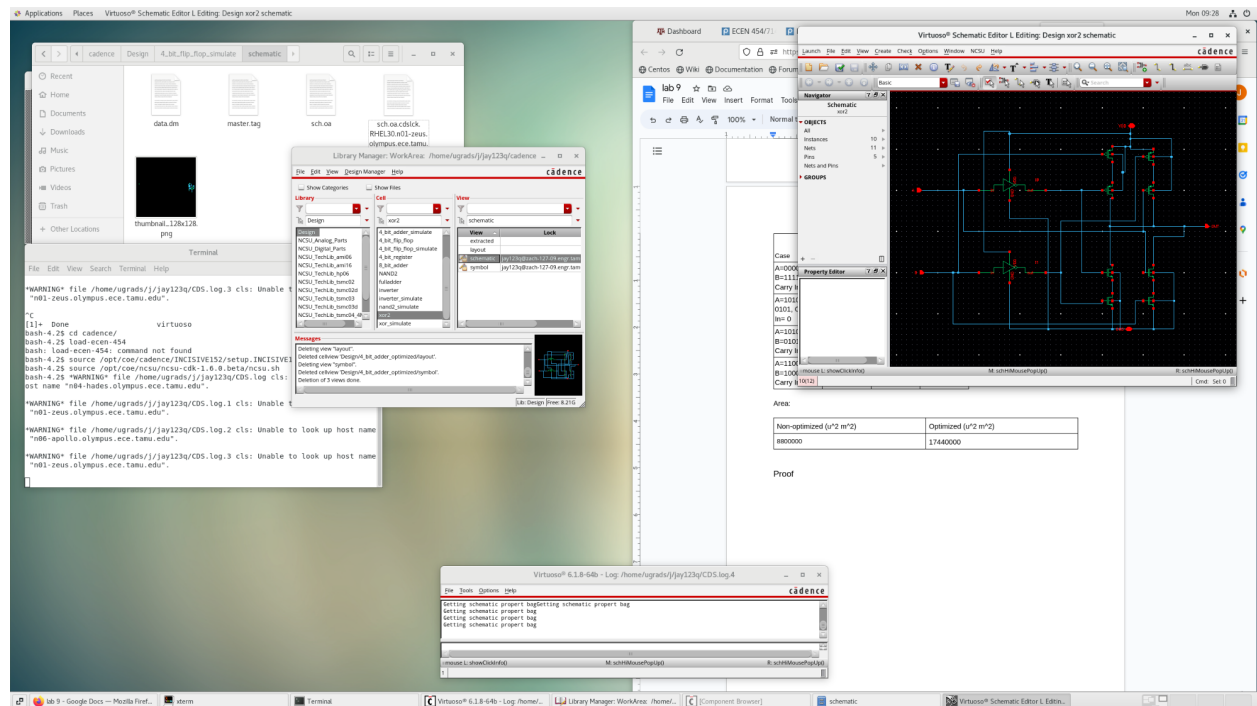

Nand

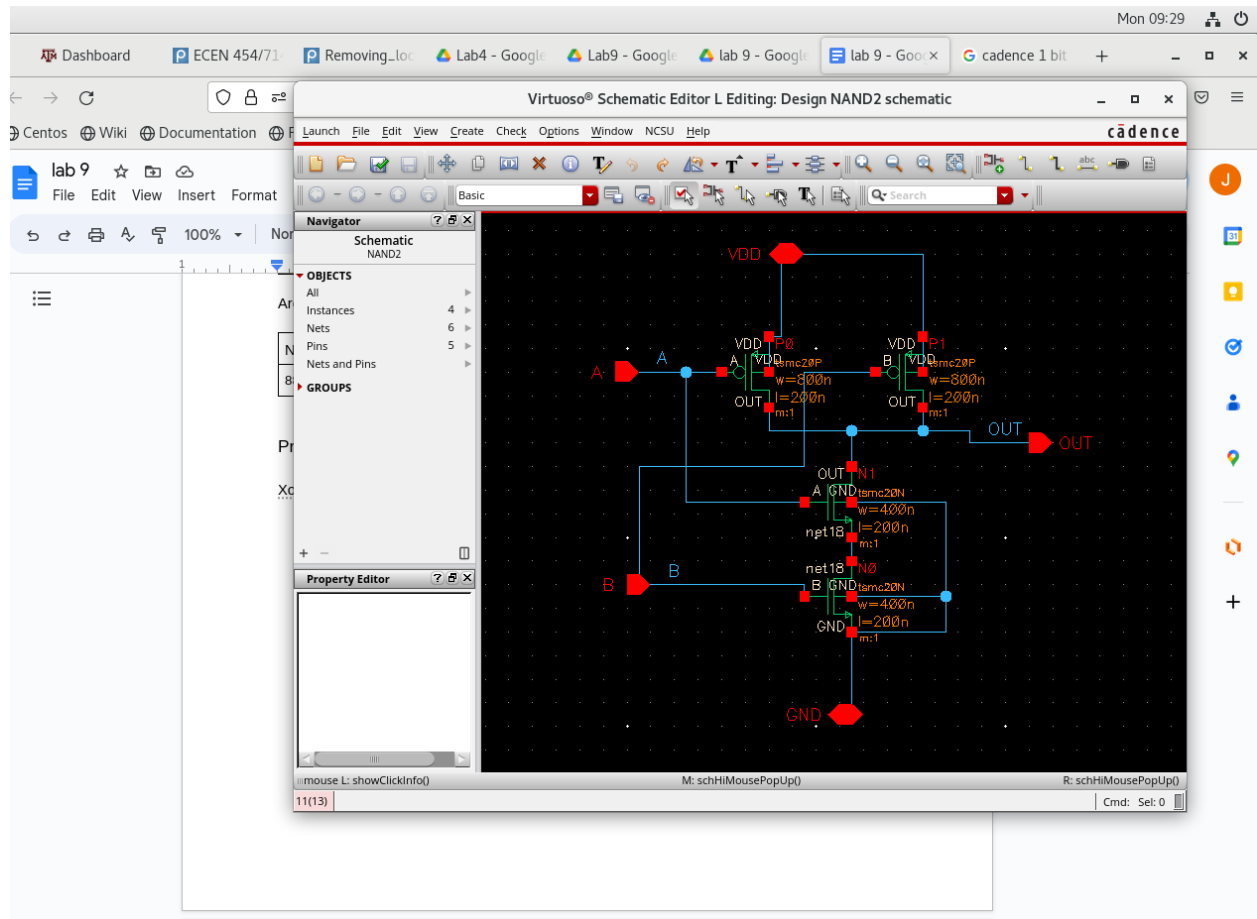

Inverter

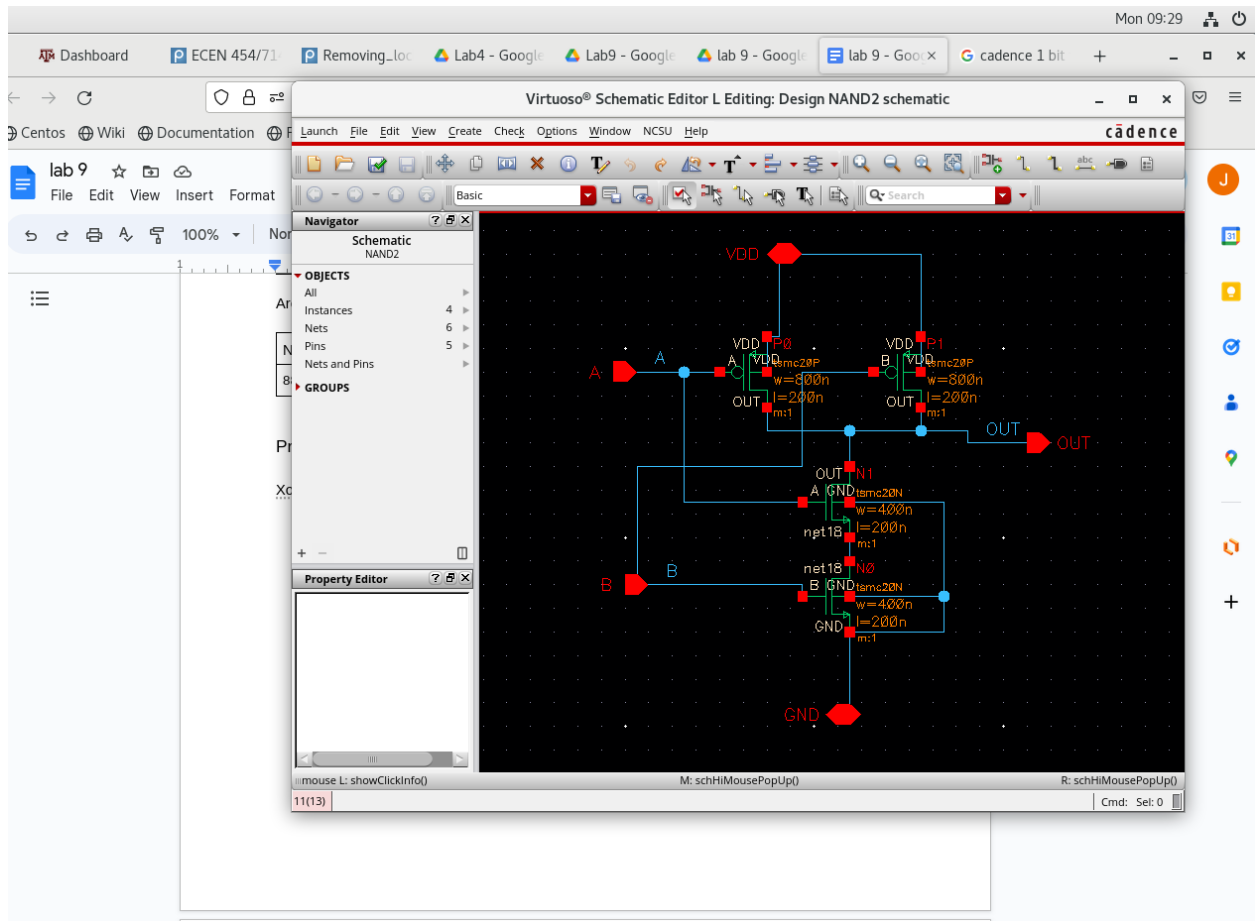

Schematic whole

MODIFIED NAND, INVERTER, AND XOR TRANSISTOR GATES TO BUILD GET PLOTS RATHER THAN REBUILD TRANSISTOR LEVEL GATES

