
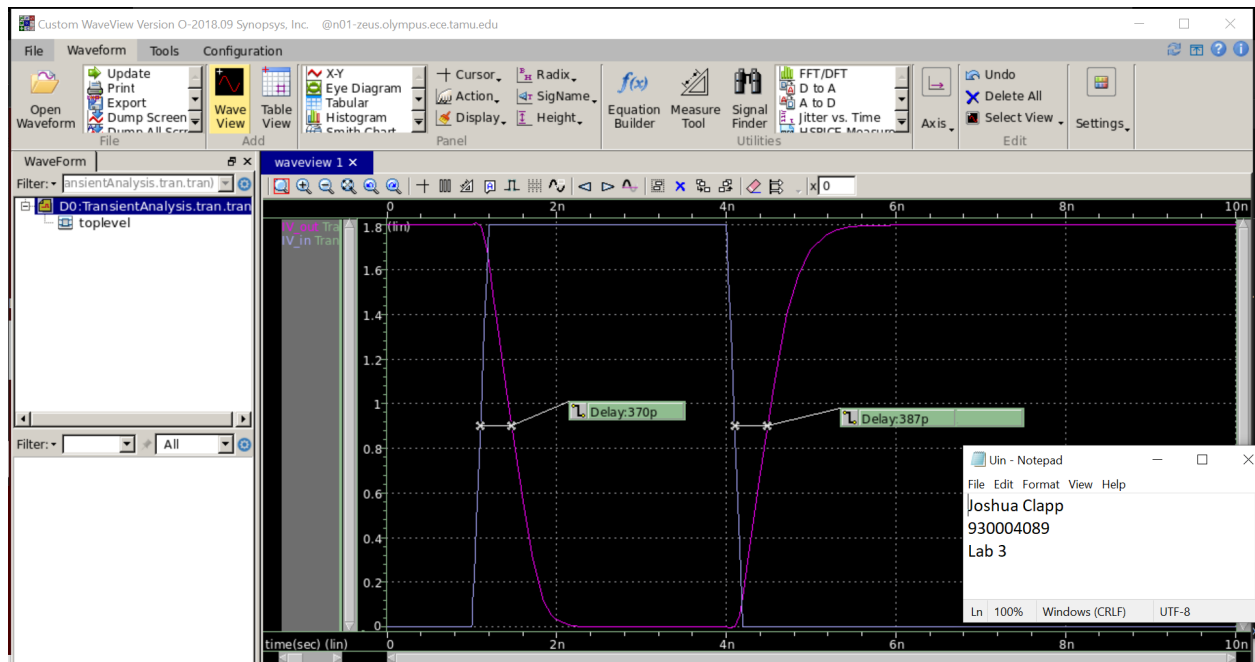


Joshua Clapp

## Inverter

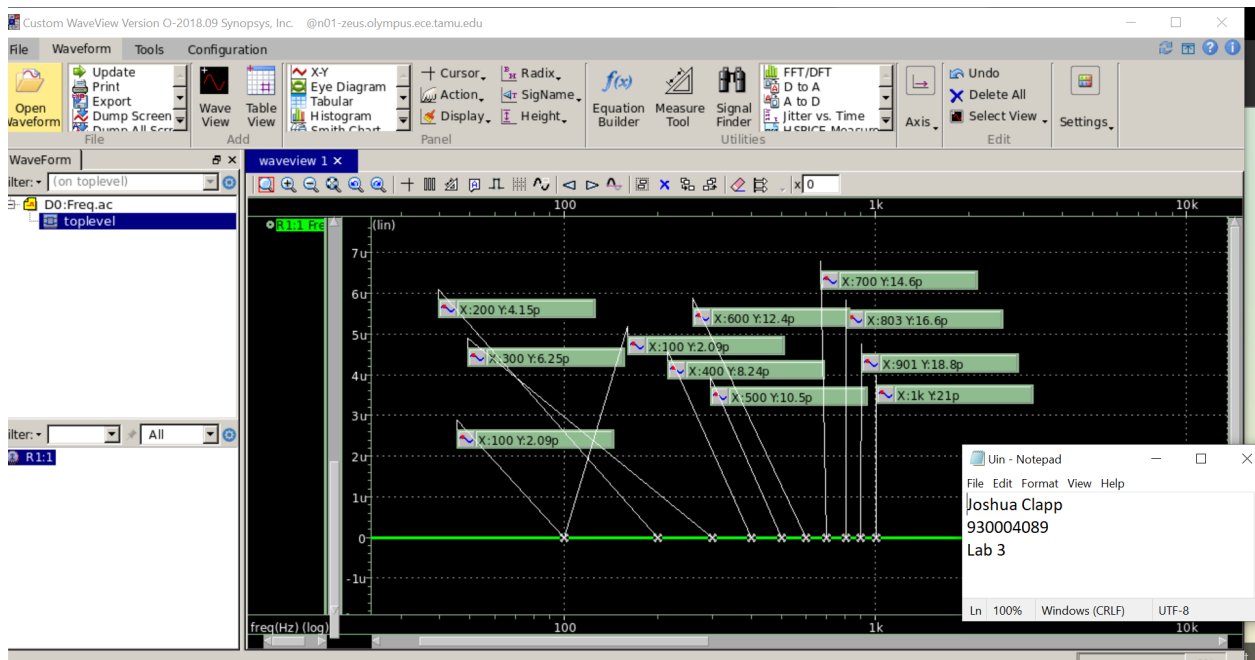

## AC Inverter



Inverter				C= I / 2*pi*f	
C (fF)	Delay R (ps)	Delay F (ps)	Error (%)	Y (uA)	X (MHz)
1	-26.4	-43.8	39.73%	2.09	100
2	-34.2	-50.7	32.54%	4.15	200
5	-53	-69.2	23.41%	6.25	300
10	-77.7	-92.7	16.18%	8.24	400
15	-98.3	-111	11.44%	10.5	500
20	-116	-129	10.08%	12.4	600
25	-134	-147	8.84%	14.6	700
30	-152	-165	7.88%	16.6	800
40	-189	-203	6.90%	18.8	900
50	-225	-238	5.46%	21	1000
60	-260	-275	5.45%	Average	Average
70	-296	-311	4.82%	13.215	550
80	-334	-351	4.84%		
				Sink Capacitance (F)	
90	-370	-387	4.39%		
100	-405	-421	3.80%	3.82E-15	

#### Inverter.spi

;Spice netlist for an inverter and a capacitor  
simulator lang=spectre

include "~/cadence/cellcharacs/model18.spi"  
include "~/cadence/cellcharacs/cell18.spi"

vgnd (gnd 0) vsource dc=0  
vdd (vdd 0) vsource dc=1.8

vpwl (IV\_in 0) vsource type=pwl wave=[0n 0 1n 0 1.2n 1.8 4n 1.8 4.2n 0]

X1 (IV\_in IV\_out vdd gnd) IV wp=0.6u lp=0.2u wn=0.3u ln=0.2u

R1 (IV\_out 1) resistor r=1  
C1 (1 0) capacitor c=100f

TransientAnalysis tran start=0 stop=10ns step=1ps  
save IV\_in IV\_out

## Simcap.spi

;Spice netlist for an inverter and a capacitor  
simulator lang=spectre

include "~/cadence/cellcharacs/model18.spi"  
include "~/cadence/cellcharacs/cell18.spi"

vgnd (gnd 0) vsource dc=0  
vdd (vdd 0) vsource dc=1.8


acinput (IV\_in 0) vsource dc=0 mag=1

R1 (IV\_in IV\_in1) resistor r=0


X1 (IV\_in1 IV\_out vdd gnd) IV wp=0.9u lp=0.2u wn=0.4u ln=0.2u

Freq ac start=1e+1 stop=1e+9  
save R1:currents

## Nand Delay Waveform

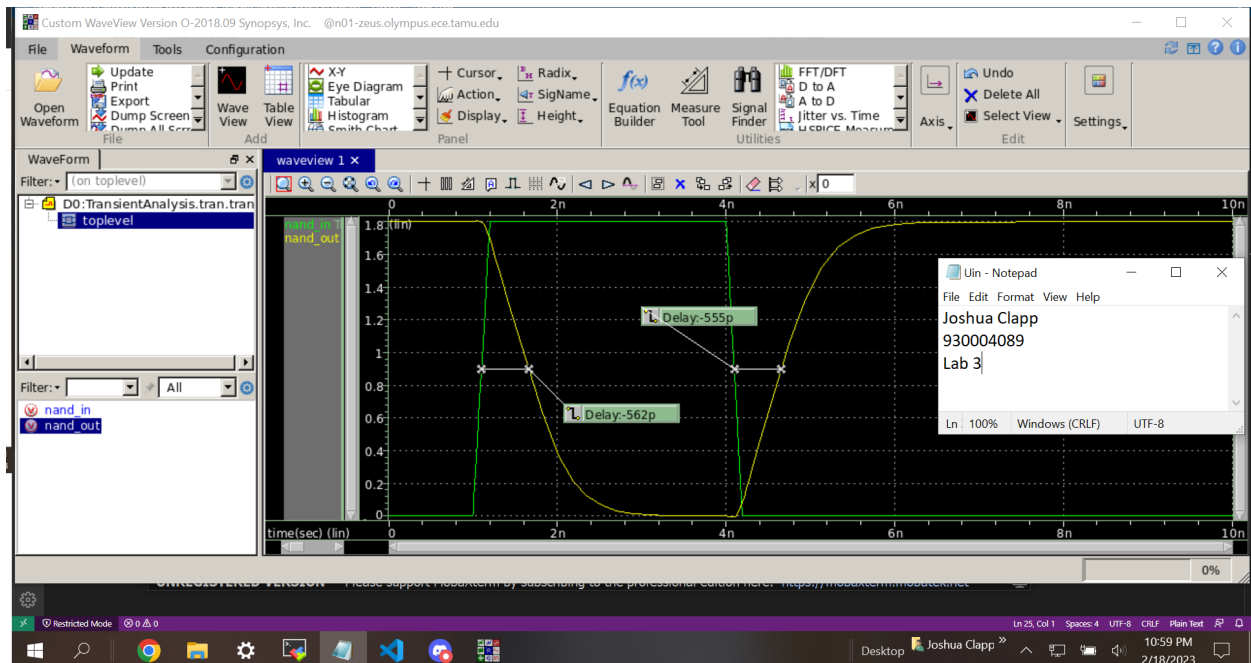

## Nand Ac

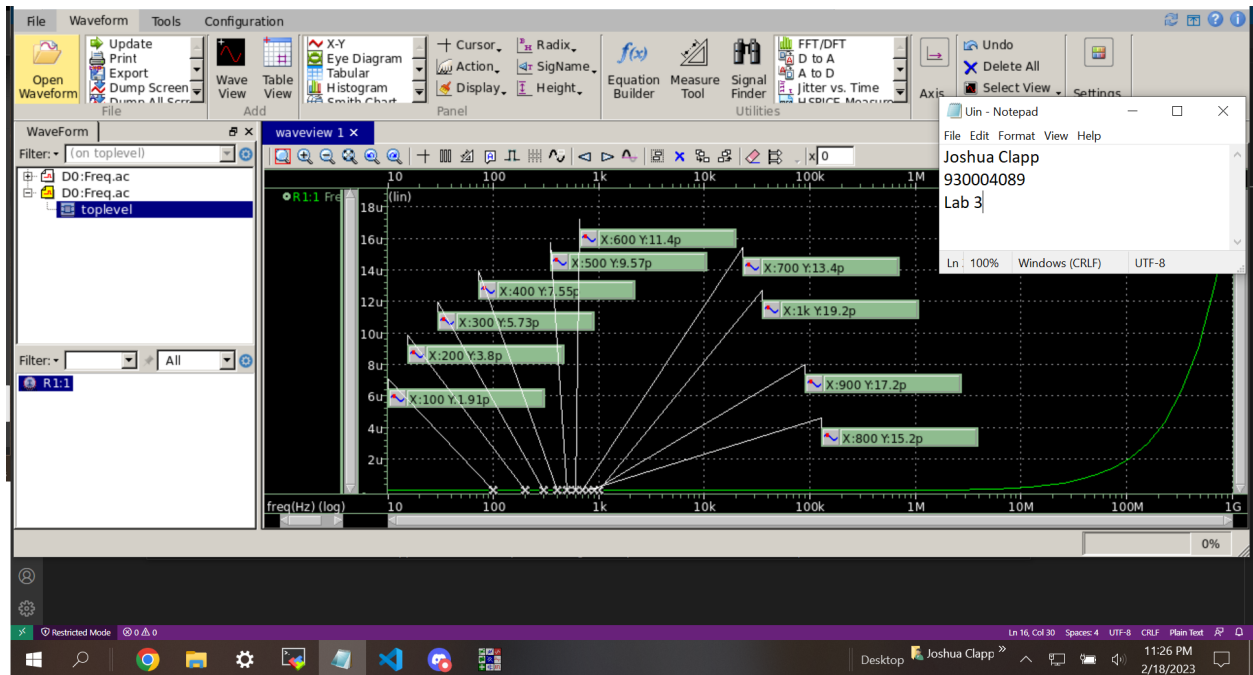

Nand				$C = 1 / 2 * \pi * f$	
C (fF)	Delay R (ps)	Delay F (ps)	Error (%)	Y (uA)	X (MHz)
1	-37.4	-54.4	31.25	1.91	100
2	-46.5	-63.1	26.30744849	3.8	200
5	-68.9	-83.9	17.8784267	5.73	300
10	-99.6	-111	10.27027027	7.55	400
15	-125	-135	7.407407407	9.57	500
20	-151	-160	5.625	11.4	600
25	-177	-184	3.804347826	13.4	700
30	-203	-209	2.870813397	15.2	800
40	-255	-259	1.544401544	17.2	900
50	-305	-310	1.612903226	19.2	1000
60	-357	-357	0	<b>Average</b>	<b>Average</b>
70	-410	-406	-0.9852216749	10.496	550
80	-460	-455	-1.098901099		
90	-510	-505	-0.9900990099	<b>Sink Cap</b>	
100	-562	-555	-1.261261261	$3.037 \times 10^{-15}$	

#### Nand\_delay.spi

;Spice netlist for an inverter and a capacitor  
simulator lang=spectre

include "~/cadence/cellcharacs/model18.spi"  
include "~/cadence/cellcharacs/cell18.spi"

vgnd (gnd 0) vsource dc=0  
vdd (vdd 0) vsource dc=1.8

acinput (nand\_in 0) vsource dc=0 mag=1

R1 (nand\_in nand\_in1) resistor r=0

X1 (nand\_in1 nand\_out vdd gnd) nand wp=0.8u lp=0.2u wn=0.4u ln=0.2u

Freq ac start=1e+1 stop=1e+9  
save R1:currents

#### Simcap\_nand

;Spice netlist for an inverter and a capacitor  
simulator lang=spectre

include "~/cadence/cellcharacs/model18.spi"  
include "~/cadence/cellcharacs/cell18.spi"

vgnd (gnd 0) vsource dc=0  
vdd (vdd 0) vsource dc=1.8


acinput (nand\_in 0) vsource dc=0 mag=1

R1 (nand\_in nand\_in1) resistor r=0


X1 (nand\_in1 nand\_out vdd gnd) nand wp=0.8u lp=0.2u wn=0.4u ln=0.2u

Freq ac start=1e+1 stop=1e+9  
save R1:currents

## Xor waveform

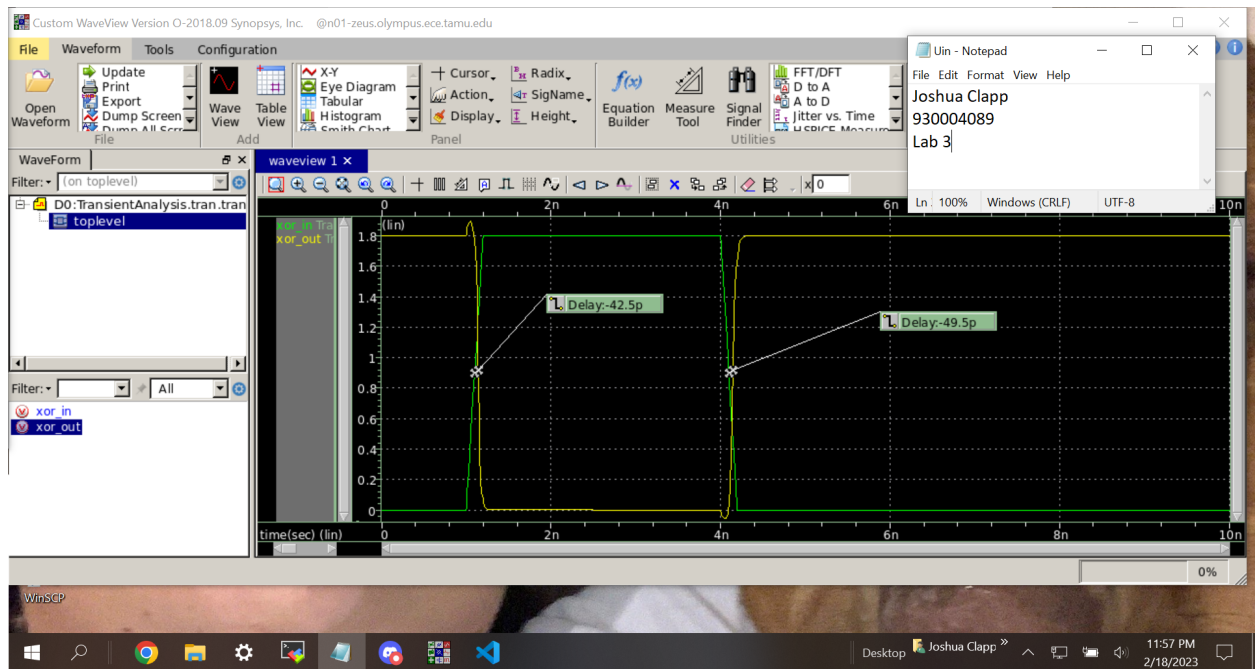

## Xor Ac

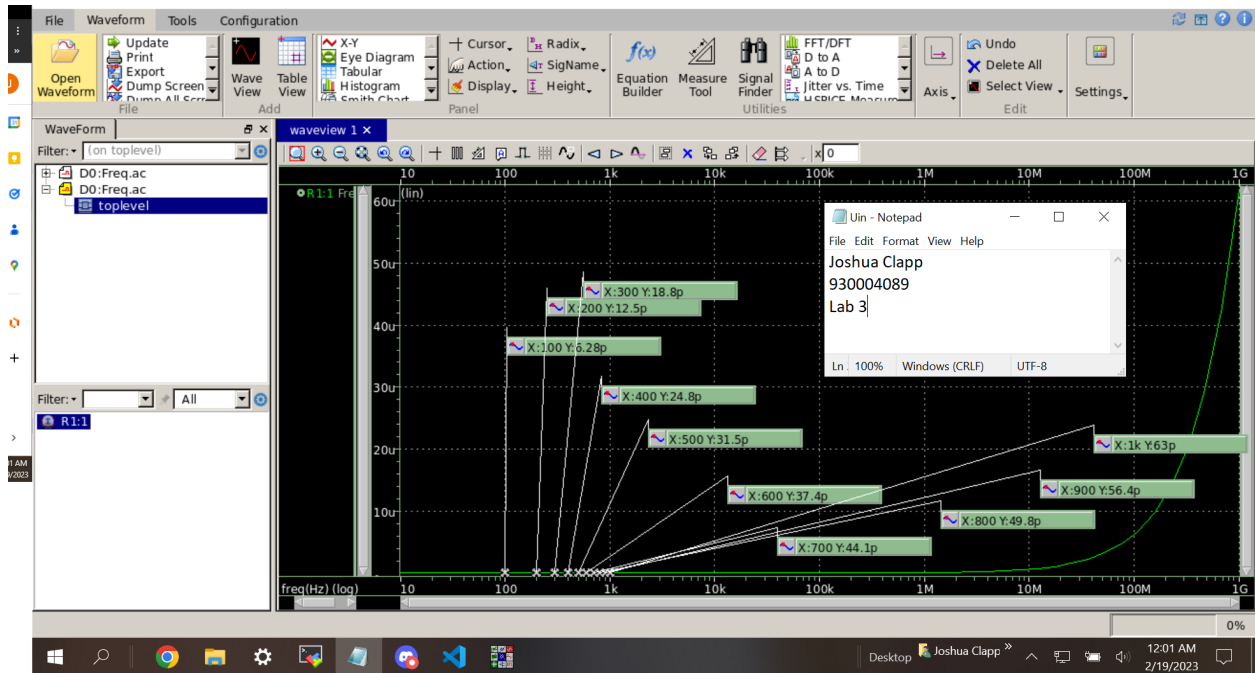

xor				$C = 1 / 2\pi f$	
C (fF)	Delay R (ps)	Delay F (ps)	Error (%)	Y (uA)	X (MHz)
1	-42.5	-49.5	14.14141414	6.28	100
2	-49.1	-56	12.32142857	12.5	200
5	-67	-74.1	9.581646424	18.8	300
10	-94.8	-104	8.846153846	24.8	400
15	-121	-130	6.923076923	31.5	500
20	-147	-157	6.369426752	37.4	600
25	-174	-183	4.918032787	44.1	700
30	-200	-209	4.306220096	49.8	800
40	-252	-261	3.448275862	56.4	900
50	-304	-312	2.564102564	63	1000
60	-355	-364	2.472527473	<b>Average</b>	<b>Average</b>
70	-407	-418	2.631578947	34.458	550
80	-458	-469	2.345415778		
90	-510	-522	2.298850575	<b>Sink Cap</b>	
100	-562	-572	1.748251748	$9.97 \times 10^{(-15)}$	

### Xor\_delay.spi

;Spice netlist for an inverter and a capacitor  
simulator lang=spectre

include "~/cadence/cellcharacs/model18.spi"

include "~/cadence/cellcharacs/cell18.spi"

vgnd (gnd 0) vsource dc=0

vvdd (vdd 0) vsource dc=1.8

vpwl (xor\_in 0) vsource type=pwl wave=[0n 0 1n 0 1.2n 1.8 4n 1.8 4.2n 0]

;X1 (IV\_in IV\_out vdd gnd) IV wp=0.6u lp=0.2u wn=0.3u ln=0.2u

X1 (xor\_in xor\_out vdd gnd) xor wp=1.5u lp=0.2u wn=0.4u ln=0.2u

;R1 (xor\_out 1) resistor r=1

C1 (xor\_out 0) capacitor c=1f

TransientAnalysis tran start=0 stop=10ns step=1ps

save xor\_in xor\_out

### Xor\_simcap.spi

;Spice netlist for an inverter and a capacitor  
simulator lang=spectre

include "~/cadence/cellcharacs/model18.spi"

include "~/cadence/cellcharacs/cell18.spi"

vgnd (gnd 0) vsource dc=0

vvdd (vdd 0) vsource dc=1.8

acinput (xor\_in 0) vsource dc=0 mag=1

R1 (xor\_in xor\_in1) resistor r=0

X1 (xor\_in1 xor\_out vdd gnd) xor wp=1.5u lp=0.2u wn=0.4u ln=0.2u

Freq ac start=1e+1 stop=1e+9

save R1:currents

### Cell18.spi

//Spice netlist for an inverter

simulator lang=spectre

subckt IV (input output VDD VSS)



```

    parameters wp=0.6u lp=0.2u wn=0.3u ln=0.3u
    M1 output input VDD VDD tsmc18P w=wp l=lp
    M2 output input VSS VSS tsmc18N w=wn l=ln
ends IV
subckt nand (input output VDD VSS)
    parameters wp=0.6u lp=0.2u wn=0.3u ln=0.3u
    M1 output input VDD VDD tsmc18P w=wp l=lp
    M2 output VDD VDD VDD tsmc18P w=wp l=lp
    M3 output input C VSS tsmc18N w=wn l=ln
    M4 C VDD VSS VSS tsmc18N w=wn l=ln
ends nand
subckt xor (input output VDD VSS)
    parameters wp=0.6u lp=0.2u wn=0.3u ln=0.3u
    M1 Aout input VDD VDD tsmc18P w=wp l=lp
    M2 Aout input VSS VSS tsmc18N w=wn l=ln
    M3 Bout VDD VDD VDD tsmc18P w=wp l=lp
    M4 Bout VDD VSS VSS tsmc18N w=wn l=ln
    M5 t1 VDD VDD VDD tsmc18P w=wp l=lp
    M6 output Aout t1 VDD tsmc18P w=wp l=lp
    M7 t2 Bout VDD VDD tsmc18P w=wp l=lp
    M8 output input t2 VDD tsmc18P w=wp l=lp
    M9 b1 Bout VSS VSS tsmc18N w=wn l=ln
    M10 output Aout b1 VSS tsmc18N w=wn l=ln
    M11 b2 VDD VSS VSS tsmc18N w=wn l=ln
    M12 output input b2 VSS tsmc18N w=wn l=ln
ends xor

```